

SPHERE

VOLUME V NUMBERS 4 and 5

May 1981

EDITORS: Jeffrey Brownstein
Roger J. Spott

Put A 6809 in the SPHERE	Brownstein	Page 1
Convert CPU Board to 2708's	Brownstein	Page 2
Bank Select Your Proms	Brownstein	Page 4
The 6800/6809 Hardware	Brownstein	Page 6
The 6800/6809 Software	Parker	Page 9
Programma 2708 Artwork	Programma	Page 12
Chip diagrams	Programma	Page 13
Programma Conversion	Programma	Page 14
The Hardware Connection	Turner	Page 16
Square Roots	Mo Beath	Page 17
The Sphere 1702A Board	Dixon	Page 18
Machine Sort for Basic	Spott	Page 26
Musical Tone Generation	Calley	Page 30
6809 Software Architecture	Mototola	Page 32
6809 Registers	Motorola	Page 33
6809 Indexed Addressing	Motorola	Page 36
6809 Indexed Post Byte	Motorola	Page 37
6809 Instructions	Motorola	Page 38

PLEASE SEND MATERIAL FOR THE NEXT ISSUE TO:

Dr. Jeff Brownstein
2 Tor Road
Wappingers, N.Y. 12590

PUT A 6809 IN YOUR SPHERE MICROCOMPUTER

Dear Sphere Users,

This article represents a very significant upgrade of the Sphere system. I have the conversion installed in mine and invite any of you to drop by when you are in the new york area. The MOD contains the following features:

One crystal controlled clock running both CPU chips.

Four to eight EPROM chips. Using 2708 or 2716 proms, four of them are active during 6800 operation while the others overlay the memory space and work with the 6809. Thus the reset and interrupt vectors which reside in the highest address prom are appropriate for each.

Only one monitor is required because the 6809 can access the I/O in the V#N#3 standard when needed. The software interrupt is re-vectored. My implementation leaves even the software interrupt alone and uses the wait for interrupt code. As described in a previous newsletter, the NMI is activated in my scheme upon execution of the wait for interrupt opcode.

The CPU of choice is selected statically with a dip switch or on the fly using one PIA B side line. This line also controls which proms are active and halts the unused processor.

For ease of removal, the adaptor board plugs into the empty 6800 socket. The CPU board will operate with the 6800 back in place but crystal clock is then not used. The adaptor board contains both CPU chips (socketed), the crystal as well as a few 7400LS chips.

The piggy back prom board plugs into one of the 1702A sockets just like the programma board. In fact it is an enhanced version to allow two banks of prom. The plans for the programma board are presented here; there is no reason that this enhancement alone cannot be implemented (but without paying out any money) on a simple perfboard. If you do not wish to use the 6809 then alternate memory banks (though still useful) are not absolutely necessary.

Besides the 6809 and some Eproms, the cost of this entire conversion is very small.

All of the features of the 6809 are supported including position independent code, multiple software interrupts, 16 bit instructions, hardware multiply, sync signal, etc. Note that the 6809E (which has an external clock and is recommended for multiprocessing and multitasking) was not used. I could not find a supplier for the 6809E. The project could use the E version with some minor wiring changes.

Although not implemented yet, It should be possible to run the system at a fast clock rate while slowing down the CPU only during accesses to external memory. The 6809 has a memory ready line on it for this purpose. Certain mask numbers of the 6809 have different requirements for synchronising the memory ready with the system clock so I this has been left alone for now.

The first part of the conversion should be the construction of the prom piggyback board. Look over the Programma plans. An artwork sample for a PC board is included for those who would duplicate the Programma board exactly. With the plans in hand, I needed some time to figure out what was the best way to proceed. Make up your mind what type of proms you will use and where you would like them addressed. Look at the address table which is presented by Programma on the plans. Because of the peculiarities of I/O locations used by Sphere, you will see that although the 2716 will give far more memory available, the smaller 2708 will slightly better utilize the memory space around the I/O ports. Because I have other memory from D000-DFFF I chose the 2708 as did most of the people who bought the Programma boards.

The main feature of the decoding is the 74LS30. I chose to place this in the spare socket of the cpu board. First I cut all traces going to all but pins seven and fourteen (the power and ground pins). If you are going to use the two memory banks you can use two 74LS30 chips mounted one on top of the other. All pins except one of the input lines are soldered together. The input pin of the top (piggyback) one is bent out. Now, the way these chips work, the proms (thru the 7442 of course) will only be selected when all of the inputs to the 74LS30 are positive. Now you can see how I implemented two prom banks. The control line for the processors and proms will either be hi or lo. It is tied to one of the 74LS30 chips input directly and to the other thru an inverter. The result is that one and only one bank of prom can be selected at any one time. It is possible to test the circuit so far by placing a scope or logic probe on the output of the 74LS30's one at a time. Verify that as you control their inputs and address memory in their range, the output goes lo (briefly). At this point the whole system is still intact with the 1702A chips in place and it still runs fine.

I now piggybacked a 7442LS on top of the existing one on the CPU board. One output from one 74LS30 goes to one 74LS42 and the other to the other 7442. You are left with a whole bunch of outputs on each 7442LS: these will go to the chip select pins of the proms according to which addresses and which kind of proms you are using. I know that this whole business with piggybacking sounds messy. Put separate sockets if you wish. The Programma board carried the 74LS30 on it. I preferred it on the CPU card to test the bank selects before removing the 1702A proms.

Construct from a piece of perfboard a piece about 2" wide by 3.75" long. If you want to use all 8 Eproms, make the board four inches wide instead. If you are going all the way to the 6809 conversion, also cut a piece of perfboard 3.75" X 3.75" and put it aside.

At your local Radio Shack you will find the necessary number of 24 pin sockets as well as a single ended 24 pin dip jumper (which will plug into the empty E35 socket of the CPU board). Most of the lines of the E35 socket will easily furnish signals appropriate for the 2708 board. Ground, -5, 12 A8 and A9 will have to be drawn from the CPU board individually. The chip selects of all the 2708 proms will also have to be brought individually to the edge of your perf board. All of the other pins of your 2708 chips are to be tied together and then to the 24 pin dip jumper according to the chart below.

<u>Signal</u>	<u>1702A (and jumper) pin</u>	<u>2708 pin</u>
A7	17	1
A6	18	2
A5	19	3
A4	20	4

Cont'd.

<u>Signal</u>	<u>1702A (and jumper) pin</u>	<u>2708 pin</u>
A3	21	5
A2	1	6
A1	2	7
A0	3	8
D1	4	9
D2	5	10
D3	6	11
D4	7	13
D5	8	14
D6	9	15
D7	10	16
D8	11	17
VCC (+5 Volts)	13,15,22,23,12	24

Note: some data sheets list data lines as D0 to D7 while others use D1 to D8. In either case the correct pin connects are here.

Now you must remember to get +12 volts to 2708 pin 19
 -5 volts to 2708 pin 21
 Ground to 2708 pin 12
 A8(E13 pin 15) 2708 pin 23
 A9(E13 pin 14) 2708 pin 22


Also remember that on the pin 20 (chip select) of each 2708 must go a lead from the correct 74LS42 and from the correct pin as shown in the table of configurations.

The theory of multiplexing the proms to allow 2 banks is as follows: We will use a PIA line to do the selecting. On top of the 74LS30 and 74LS42 chips (or next to them etc) we will connect duplicate chips. Programma mounted its 74LS30 on the conversion piggyback board but I put mine in the spare socket of the CPU board. According to Programma's circuit, the 74LS30 has pins 1,2 and 3 tied together. If any one of these pins were not tied to +5, no chip select could occur through that 74LS30 and its associated 7442. What I do is drive one of the 74LS30 's pin 1 with the CONTROL signal from the 6809 board. The other 74LS30 pin 1 is driven through an inverter. On my CPU board, E40 pin 5&6 was available and already had a 1K resistor (R17) tied to the output. This arrangement assures that if the CPU board is used without the 6809 piggy, the prom bank for the 6800 is the one that remains selected. Now it should be clear that one and only one bank of prom on the CPU board will be able to be selected at any time and that which one is dependent upon CONTROL line which is toggled by a PIA line. Control line also serves to select 6800 or 6809 processors. If we try to have only one bank of prom, it will be impossible to have the interrupt vectors and also the reset vector work correctly for each processor. Also, the 6800 monitor will not execute when the 6809 is up.

Study the Programma 2708 LOGIC LAYOUT diagram. After the CPU board back side jumpers are done, make certain that A13, VMA&02, R?W, A14, A15, +5 and ground all get to the 74LS30 correctly. According to the program's decode chart, select your desired addresses for the proms. On my system E35 from the second 74LS42 goes for FC00 to FFFF in the 6809 mode and therefore hangs on pin seven of that second 7442. The pin 20(CS) of the prom is directly connected to pin seven of the extra 74LS42. My monitor for 6800 mode is connected with its CS tied to pin seven of the other 74LS42. Now the other two proms may be tied to any other combination of addresses on either 7442LS as desired. Although I have not physically added four more prom sockets yet, you should be able to see that there exists a potential of two banks with four 2708s in each. One bank will run when CONTROL is hi while the other bank will be active when CONTROL is lo.

The best thing about this arrangement is that when you are done it is easily tested. Do this before continuing to 6809s.


See "Jumper Layout" + TABLE

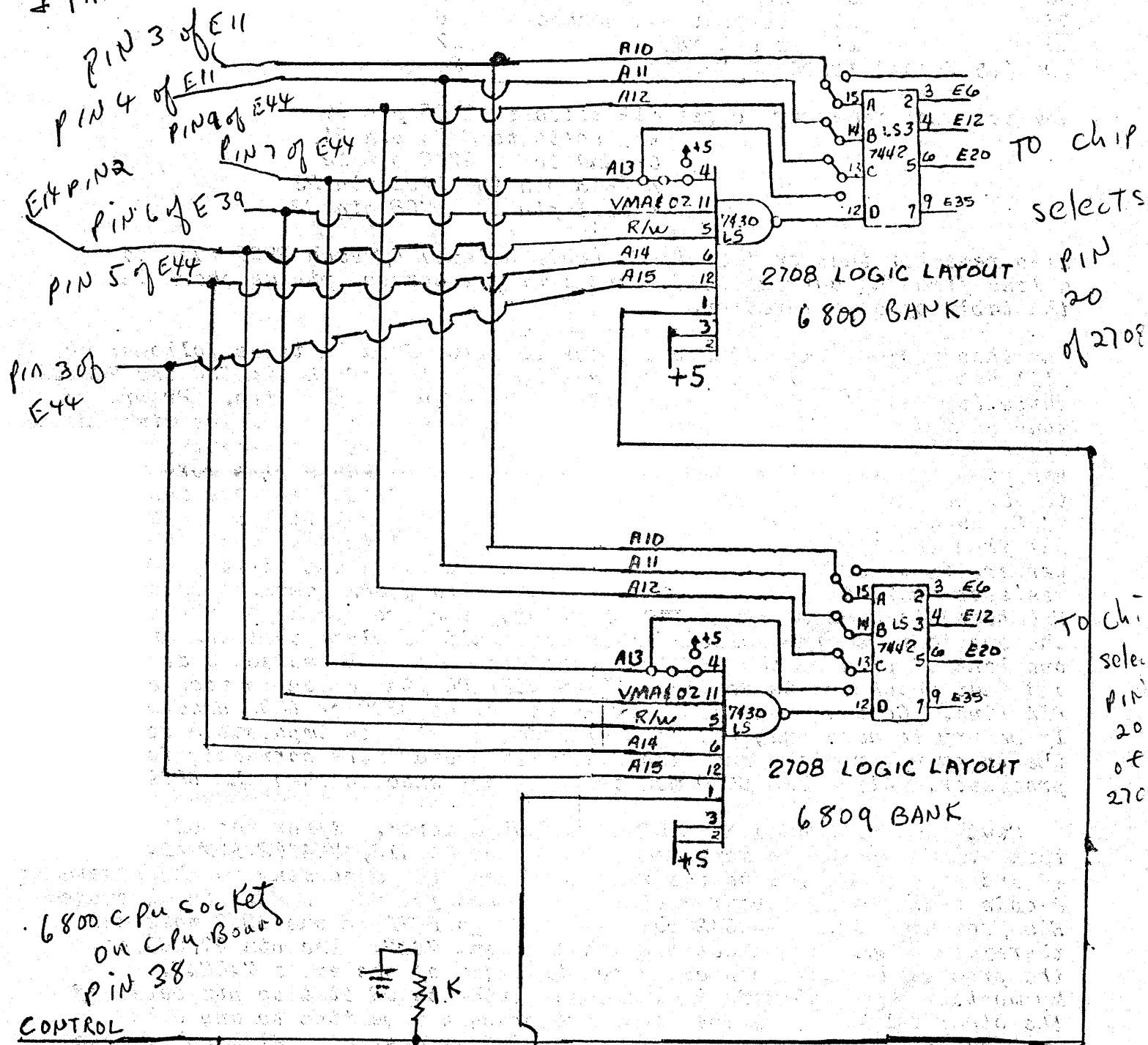

6800 CPU socket ON CPU Board PIN 38


CONTROL

 = 6800 ON
 = 6809 ON
 (Disable ground from PIN 38)



To test your prom 2708 setup merely insert a 2708 in each socket. If you blast one containing the V3N monitor, you first can set that one up as the highest address of the 6800 prom bank. Other proms may be then inserted in the other available sockets and their contents read with the debugger. Now connect +5volts to CONTROL line and the monitor should run perfectly in the highest address socket of the other bank. When all of this runs fine you are ready to go on to the 6809 adaptor. I believe that Warren Weimer has access to a few Programma piggyback PC boards (although I built mine from scratch). Whether the Programma board is used or not, you will still have to add one 74LS30 and one 74LS42 at least. Actually, I changed the original 7442 to a 74LS42 for good luck.

 It is necessary next to procure a 12" 40 pin double ended jumper. This part may be obtained by mail from DigiKey or Jameco. On the square per-board lay out three 40 pin (female) sockets. My layout is as below:



At this point I recommend that the 6800 socket S2 and the cable socket S1 be wired together pin for pin except for the unused pins 35 and 38. We will use them to allow two signals to transverse distance between our CPU and adaptor board. 38 will carry CONTROL while 35 will take the E clock from the adaptor board to the new CLOCK SWITCH (more about that later). There is no reason that the following connections cannot be made to the 6809 socket at this time (do not install the 6809 yet though):


- ALL 8 DATA lines
- ALL 16 ADDRESS lines
- R/W
- RESET
- VCC
- VSS

If you install the 6800 in the socket of the adaptor board it had better work. At least if it doesn't you have just a problem for solution with an ohmmeter. When all is well, continue on next page.

Now the next consideration is the clock circuitry. The 6800 chip gets clock pulses into it; two phases yet! The 6809, on the other hand, puts out clock pulses on the E and Q lines and crystal controlled. A quartz crystal is divided down in frequency by four. **ARRRGH!!!!!!**

Here is a way to reconcile all of this: E45 is the Sphere clock generating chip. It has two sections. (SEE SCHEMATIC) the right side generates $\phi 2$ and then triggers the left side which generates $\phi 1$ and then triggers the right side again. If we could break this cozy little loop and feed the right half with the E clock from the 6809, all would run as before including the left side still generating $\phi 1$ for the 6800. Memory refresh would occur exactly as before and there would be a smooth transition from processor to processor since the same clock would run everything.

Now let's do it. Bend up pins 12 and 13 of E45 so they are not in the socket. Mount a 4unit dip switch below E51. We will make provision for running the old clock in the event that the 6809 board is ever removed. Also note that a little capacitor and voltage divider was necessary to force the right side of E45 to have the right input swing. The circuit is below. When SW1 and SW2 are closed the old clock works. When these are open and SW3 and SW4 are closed the 6809 clock will run the system. By the way, the divider resistors and caps have been tested & run ok for frequencies between 500KHz. and 1MHz. Different values may be needed if you pass these limits.

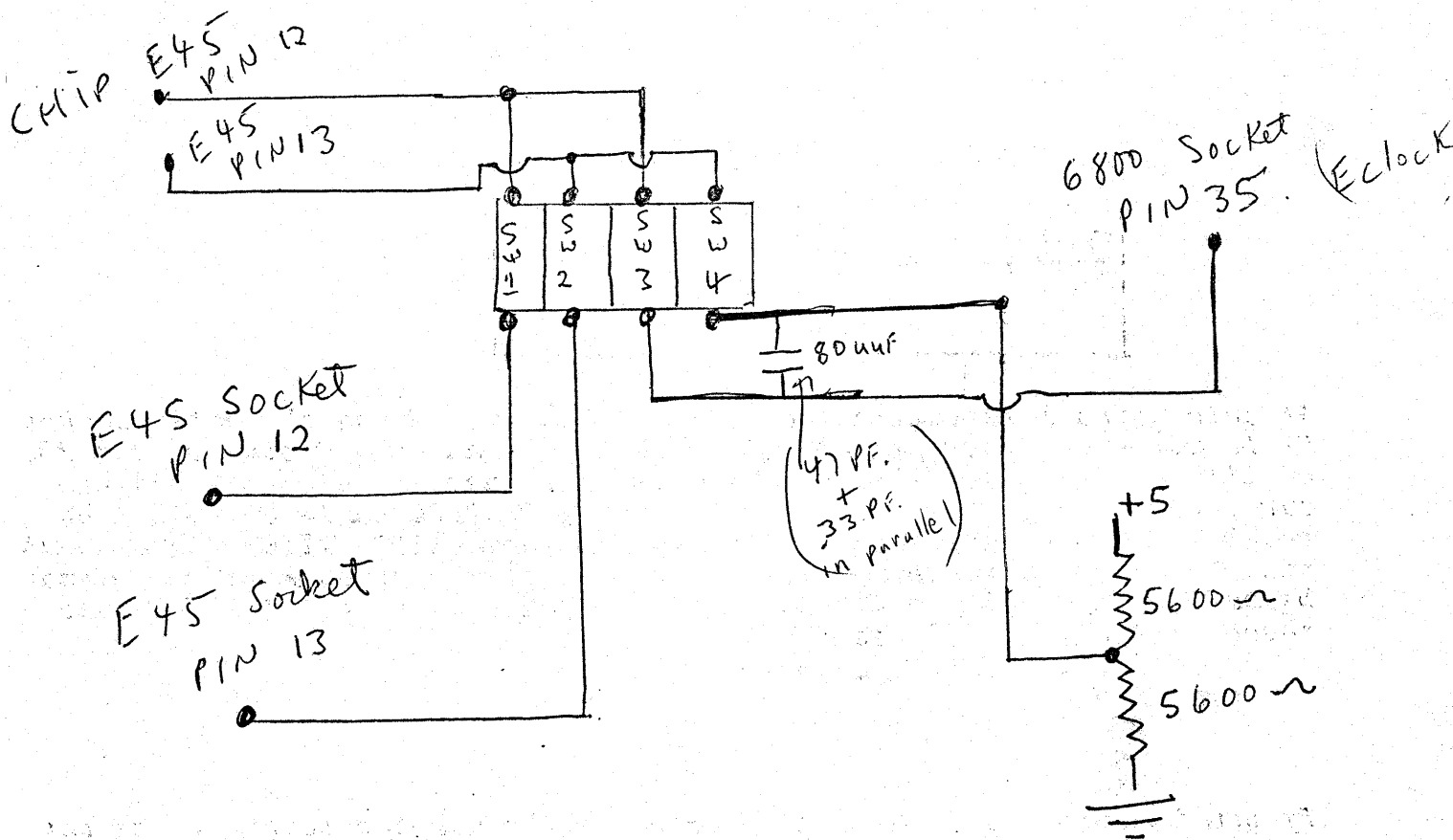

While you are near E45 you might as well change R13 (above E45) to 11K or less to enhance memory write operations. (see previous newsletters).


At this point the 6800 should still work while on the adapter board as long as SW1 and SW2 (see above) are closed. Now there are more

wiring changes to be made before the 6809 can be plugged into its socket. They are on the adapter board only.

1-Install crystal. The final project works well with a 4.000 MHz. quartz crystal. This allows both the 6800 and 6809 to run at their rated clock frequencies. I recommend that during debugging of this project, a lower frequency crystal be substituted. Why add complications? You know the system runs ok at 6 or 7 KHz. so a 3MHz crystal would be ideal at the beginning. I actually used a 2.0 MHz. one because it was all I could find around. The crystal is connected between pins 38 and 39 of the 6809 socket. You should run a 27 Pf. capacitor from each crystal lead to ground. Try to keep this wiring short as possible.

2-The 6809 E Clock. This is the same as the 6800 $\phi 2$ clock. Run a wire from 6809 socket (S3) pin 34 to pin 35 of the dip cable connector socket. Voila! Cable connector socket is S1.

 
3-DMA BREQ of 6809. Run a line from 6800 S2 pin 39 (TSC) to the input of an inverter (74LS04). The output of the gate goes to DMA BREQ of the 6809 S3 pin 33




4- FIRQ of the 6809 Just connect pin 4 of the 6809 to +5 thru a 1K resistor.


5- MREADY of the 6809 Just connect pin 36 of the 6809 to +5 thru a 1K resistor.

 6- VMA The old 6800 VMA is added and inverted with the 6809 BA to form the new system VMA. It works!!!



7-BA

 

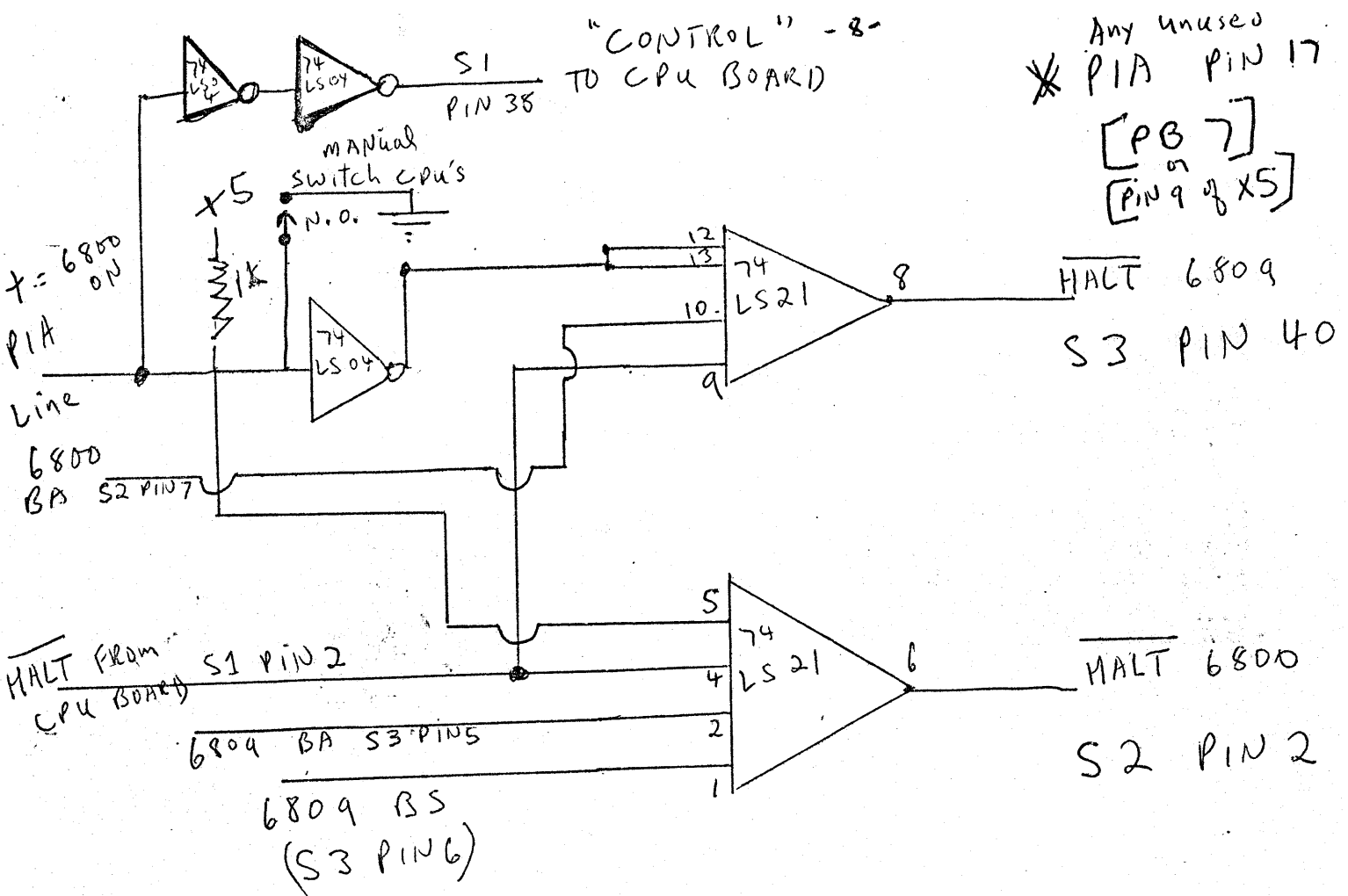

Above is the circuit which, on the command from a PIA line, causes one, the other, or, during refresh, both of the processors to halt. A manual SPST switch is incorporated to allow easier troubleshooting and to provide a way for the machine to be locked into the 6809 mode if desired.

The software half of this project requires some RAM or ROM which is outside of the bank select areas. In other words, this program must always be on line. In my system it resides in some ROM at D000. Also, correct transfer vectors must be installed in the highest memory (FC00-FFFF) ROM for each bank. The correct tables of jumps will be given later. The only requirement for the old V3N monitor rom is that the software interrupt be vectored to handle the transfer from 6800 to 6809. The idea is that upon encountering a 3F the interrupt handler routine does a few housekeeping things and then switches the PIA line thus switching processors. The registers of the 6800 are transferred to a stack from which the 6809 retrieves them.

Personally,* I never cared for dedicating the software interrupt to the above use. Some few newsletters ago I described a way of hooking the BA line of the 6800 to the NMI line. Now upon receiving a WAI or in object code 3E, the essentially same thing happens as with a 3F. Most of us have no other use at this time for the NMI line or the wait for interrupt instruction anyway. If you do it with NMI, all of your old software will have the breakpoint available as before. Another way to solve the problem might be to vector the software interrupt to RAM and have that next jump in RAM set one way for breakpointing and another when using the 6809 processor.

THE SOFTWARE 6800/6809 SWAPPER (a Bside wire will go from
your PIA pin 17 to
the new hardware)

PIADATA	EQU	F18B	
PIASTAT	EQU	F188	A side is only used as register to see if cold
PIADIR	EQU	F18A	
SP6800	EQU	C382	put it where you wish in RAM
SP6809	EQU	C05C	" " "
STACK09	EQU	C028	" " "

Vectors for 6800 Hi PROM FC00-FFFF (contains v3N monitor).

FFF8	0104	IRQ	same as before
	0100	SWI	If you decide to shift processors with 3F then E932
	E932	NMI	WAI (3E) causes NMI which jumps to SWAPPER routine
	FC00	RESET	same as before

Vectors for 6809 Hi PROM FC00-FFFF (rest of prom available for user)

FFF0	RESERVED by MOTOROLA 0000		
FFF2	E998	SWI 3	use for something else later
FFF4	E998	SWI 2	use for something else later
FFF6	E992	FIRQ	set like reset for now
FFF8	E992	IRQ	" "
FFFA	E998	SWI 1	for now any of the SWI's will switch you to 6800
FFFC	E992	NMI	use for something later
FFFE	E992	RESET 09	

ACTUAL SWAP ROUTINE (must not reside in banked proms)

	ORG	E932	
7D	F188	TST	PIASTAT Is it cold start? SWI COLD START
26	08	BNE	GO do not reset stack unless cold start
CE	C01D	LDXI	STACK 09-11
FF	C05C	STX	SP 6809
6F	03	CLR	CLRX,3
GO	BF	C382	STS SP 6800 SWI WARM START!
	FE	C05C	LDX SP 6809
	32		PULA
	A700	STAX,0	PULL DATA FROM
	32		PULA 6800 STACK AND
	A702	STAAX,2	STORE IT ON 6809
	32		PULA STACK.
	A701	STAAX,1	
	32		PULA
	A704	STAAX,4	
	32		PULA
	A705	STAAX,5	
	32		PULA
	A70A	STAAX,10	
	32		PULA
	A70B	STAAX,11	
	7F	F18A	CLR PIADIR SWAP PROCESSORS
	7F	F18B	CLR PIADATA
	86	FF	LDA#FF
	B7	F18A	STAA PIADIR
	B7	F18B	STAA PIADATA
	4F		CLRA
	B7	F18A	STAA PIADIR
	01		NOP WAIT HERE (do not try to omit this NOP)
	FE	C05C	LDX SP 6809
	A60B	LDAAX,11	TRANSFER FORM 6809 STACK
	36		PSHA TO 6800 STACK
	A60A	LDAAX,10	
	36		PSHA
	A605	LDAAX,5	
	36		PSHA
	A604	LDAAX,4	

Swapper software continued.

36 PSHA
A601 LDAAX,1
36 PSHA
A602 LDAAX,2
36 PSHA
A600 LDAAX,0
36 PSHA
3B RTI AND RETURN

RESET 09 10FE INITIALIZE THE 6809 STACK and PULL EVERYTHING
C05C (this is 6809 code)
35FF

SWI 1 10FF SAVE STACK POINTER AND SWAP PROCESSORS
C05C BACK TO 6800
86 FF (this is 6809 code)
B7 F188
7F F18B
7F F18A
12 3B Do not try to eliminate the NOP

Actual address of RESET 09 was E992
Actual address of SWI 1 was E998

Notes: Besides getting the correct vectors into each prom, the software is relatively short but do not be deceived by its apparent simplicity. Be careful if you try to rewrite it. It is possible to cut two thirds of it away by coding the largest part in 6809 instead of 6800 but we have not debugged this yet. Except for the prom vectors, the thing may be debugged and played with in RAM. The prom vectors may also be vectored to ram where you can modify them if you want to ~~fix~~ play around.

There is a need for the swapper program to reside outside of the banked proms. I had a ~~XXXX~~ 2716 from E800-EFFF so I put it in that. Here is another possibility: Once you have 2708's in the Programma or home brew piggyback, the prom on your SIM will be unplugged. The routines will (should) be in the prom which now is at E20. What to do with that empty socket?? It might be possible, after re-addressing the socket slightly, to try to find one of your 1702A proms which will run ok at 1MHz. This is easy to try (and nevermind what is in the prom). Unplug your 2708 at E20 and stick each prospective 1702A into the prom socket on the sim board. You might hit it lucky. I could burn in your 1702A with the swapper code. If none of the 1702a's will work, you could put a 2708 in and rewire the socket as well as the addressing circuitry. Of course, you could keep the swapper stuff all in RAM if desired or you could experiment by trying to divide it up and put it in the banked proms (good luck).

Gentlemen, this entire thing works very well. I could build another prototype very quickly though it took literally hundreds of hours to get the first one up. Nothing ever works right the first time for me. Please forgive my writing style as I really have not got time to rewrite this article over. I will help anyone who decides to go

- 11 -

More Notes on the 6809 conversion.

On the previous page I suggested that the unused 1702A socket on your SIM board might be an easy place to put the SWAPPER routines. Well, I just tried it out. Sure enough, the first junky old surplus 1702A worked fine. It executed perfectly in my system with the 1MHz. crystal clock. That is not to say that every 1702A will work but I bet that most will. According to where you have unused space in the memory map, a few jumpers could re-address that sim board prom socket!

I never gave you a test program to run 6800/6809 so here's one.

3E Wait for interrupt. If you utilized software interrupt then this byte will be 3F instead.

6809 routine

3F go back to 6800

```
0200 BD FC4A   GET A character (key board)
0203 3E   use WAI to goto 6809
0204 4C   Acc. A is incremented by the 6809
0205 3F   goback to 6800
0206 bd FCBC output the character
0209 7E 0200 LOOP
```

This little test routine will print out the ASCII character which is one greater than the one typed in by the keyboard.

P.S. The absolute cheapest way to go 6809 is to buy a PERCOM adapter board for 39 dollars. Use the clock circuit to feed the E clock of the 6809 into your 8602 circuit just as I did for this conversion (capacitor and voltage divider and all). Now select 4 1702a proms which will work a 1MHz. and put a monitor into them (ours but written in 6809 code or PSYMON) Psymon comes as a listing with your Percom kit. I bought the Percom kit because it was the only place that I could find a 6809! Board is left over! Of course the thing is 6809 only unless you want to pull the cpu out of its socket and switch back and forth every time. No thanks!


HELP!!!!!!!!!!!!

Hey! we need an assembler for the 6809 badly. Probably we could modify a 6800 assembler but we need a good algorithm for the "post byte" which the 6809 uses. Motorola makes an editor and assembler on cassette for their MEK6809D4B kit (sort of like the old D2 kit.).





The part number of the cassette is: MEK6809AC

When the local Motorola office heard that I am not with any big company, they would not help me.


PROGRAMMA PIGGYBACK BOARD ARTWORK

 


1

   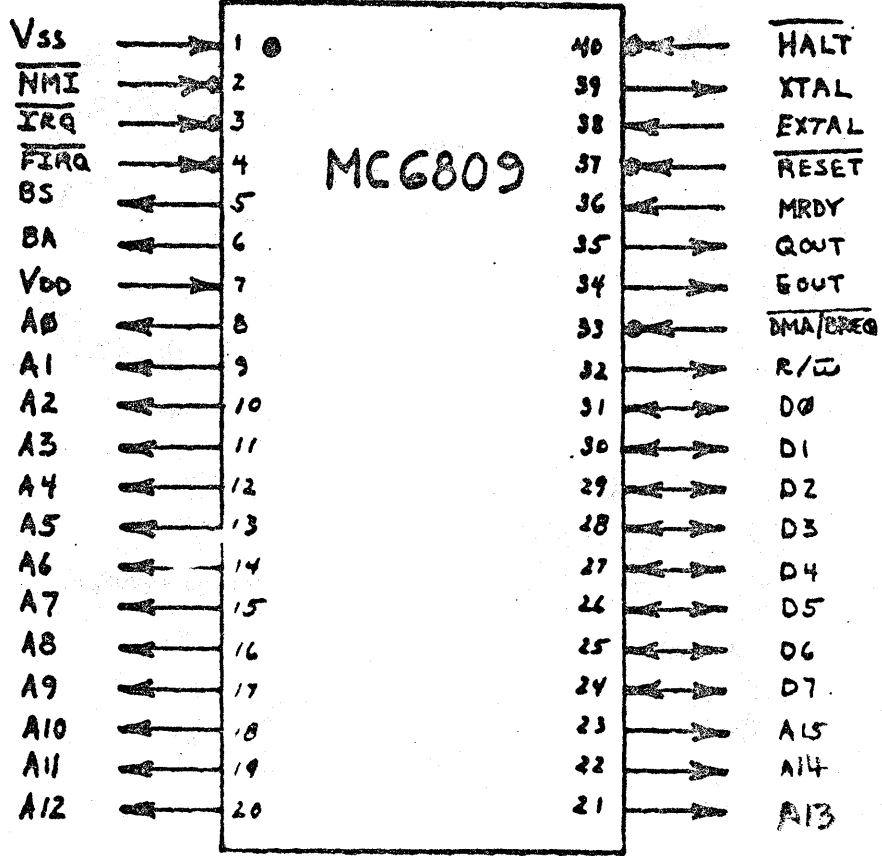

 
5420/7420(J),(N); 54H20/74H20(J),(N);
54L20/74L20(J),(N); 54LS20/74LS20(J),(N),(W);
74S20(N)



 5421/7421(J),(N); 54H21/74H21(J),(N),(W);
74S21(N)




 5411/7411(J),(N); 54H11/74H11(J),(N);
54L11/74L11(J),(N),(W); 54LS11/74LS11(J),(N),(W);
74S11(N)




5404/7404(J),(N); 54H04/74H04(J),(N);
54L04/74L04(J),(N); 54LS04/74LS04(J),(N),(W);
74S04(N)

-14-
 ESCO to E600


 


STRAPING FOR INTEL 2716

 
(D) CUT Etch wire X marks the spot (6 X's)
 (input in jumper)
 (clock lines) (6 jumpers)



PIN CONFIGURATION

  

2716 Address Range	Bin number	Binary Code	Decode number	2708 Address Range	Present Hook 4P
		A B C D			
C000 - C7FF	1	0 0 0 0	0	E000 - E3FF	*
C800 - CFFF	2	1 0 0 0	1	E400 - E7FF	
D000 - D7FF	3	0 1 0 0	2	E800 - EBFF	E6
D800 - DFFF	4	1 1 0 0	3	EC00 - EFFF	E12
E000 - E7FF	5	0 0 1 0	4	F000 - F3FF	
E800 - EFFF	6	1 0 1 0	5	F400 - F7FF	E20
F000 - F7FF	7	0 1 1 0	6	F800 - FBFF	
F800 - FFFF	9	1 1 1 0	7	FC00 - FFFF	E35
N/A	10	0 0 0 1		N/A	

 

2708 LOGIC LAYOUT


F000

UPDATED 3/21/78



Jumper Layout 2/8/78

-5

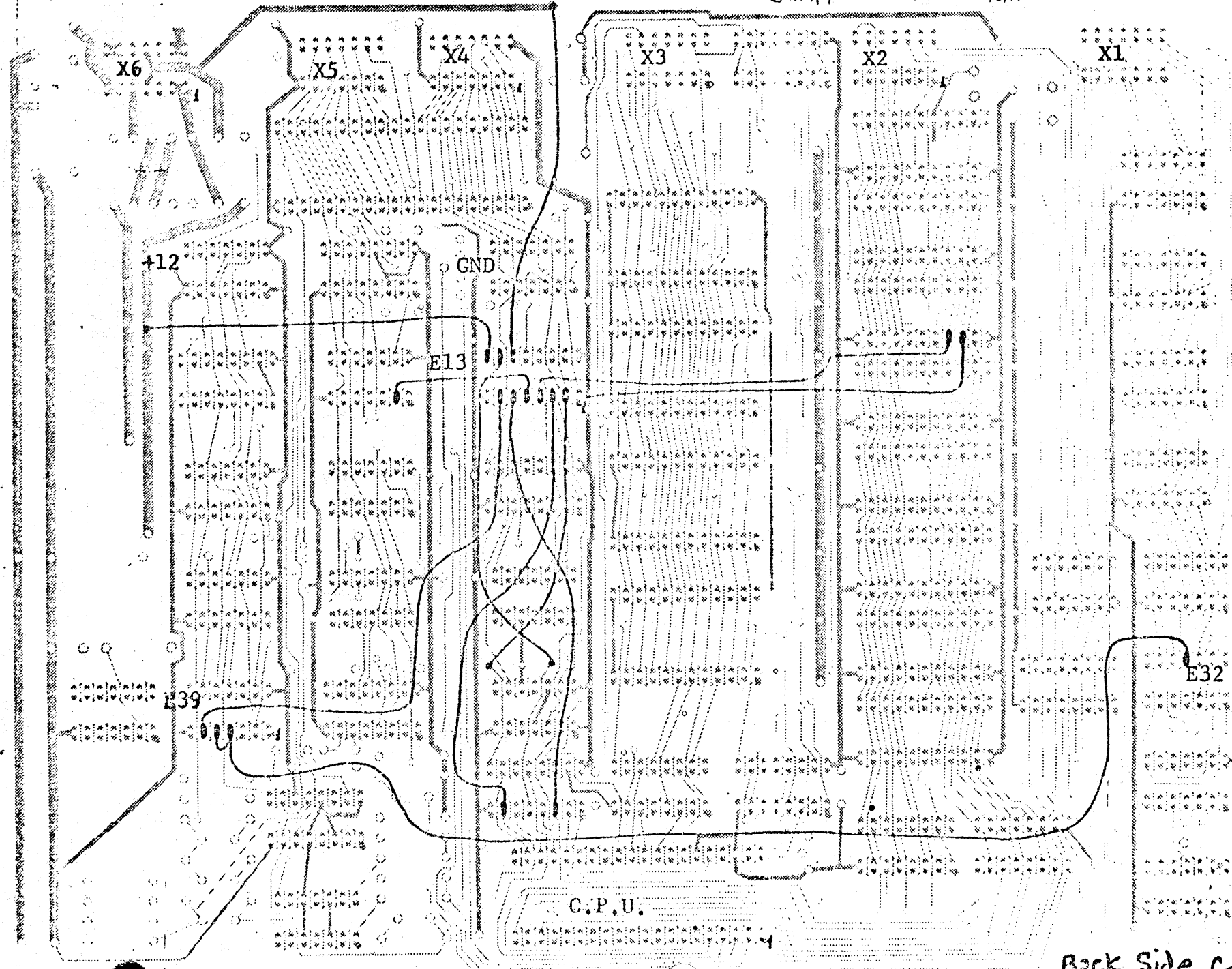

Pin #	E13 fun.
1	= A10
2	= A12
3	= A13
4	= A11
5	= R/W
6	= A15
7	= VMA&02
8	= GND
9	= +12
10	= A14
11	= -5
12	= n/a
13	= GND
14	= A9
15	= A8
16	= +5


-15-

C.P.U.

Back Side CPU #1

The Hardware Connection

by Hugh Turner

 

24 PIN MEMORY EPROMS, PROMS & RAMS

DEVICE	TYPE	MANUF	SIZE	PIN 18	PIN 19	PIN 20	PIN 21
2708	EPROM	TI	1K x 8	PROG	+12V	CS* (PE)	-5V
2508	EPROM	TI	1K x 8	PD/PROG	NC	CS*	Vpp
2758	EPROM	TI	1K x 8	PD/PROG	AR	CS*	Vpp
3628	PROM	INTEL	1K x 8	CS4	CS3	CS2*	CS1*/PROG
4801	RAM	MOSTEK	1K x 8	CS*	NC	OE*	WE*
4118	RAM	MOSTEK	1K x 8	CS*	L*	OE*	WE*
4008	RAM	TI	1K x 8	CS*	AR	OE*	WE*
2716	EPROM	INTEL	2K x 8	CS*/PROG	+12V	A10	-5V
2516/2716	EPROM	TI	2K x 8	CS*/PROG	A10	OE*	Vpp
3636	PROM	INTEL	2K x 8	CS3	CS2	CS1*/PROG	A10
4802/4016	RAM	MOS/TI	2K x 8	CS*	A10	OE*	WE*
2732	EPROM	INTEL	4K x 8	CS*	A10	OE*/PROG	A11
2532	EPROM	TI	4K x 8	A11	A10	PD/PROG	Vpp
4732	PROM	TI	4K x 8	A11	A10	CS	CS*/PROG
4764	PROM	TI	8K x 8	A11	A10	S*/PROG	A12

This is the first in a series of articles which I hope you will find useful if you do any building or designing. These data sheets can be copied or cut out and kept in a reference notebook.

Memory devices using 24 pins only have 4 pins which are used to define the device, the rest of these pins are all the same.

Please feel free to contact me if you have any hardware data you would like to see in this collection. I can be reached at 276-1638.

CS*/S* = Chip Select (Low)
 OE* = Output Enable (Low)
 WE* = Write Enable (Low)
 PD = Power Down
 PROG/(PE) = Program Enable
 Vpp = +25V (Program Voltage)
 L* = LATCH (LOW)
 AR = Array: If True Output VI0
 If False Output VI1

- 91 -

EDN Software Note #55

6800 routine extracts square roots

Mike McBeath
Microface, Torrance, CA

The algorithm shown in the figure determines a 16-bit square root for any number up to 64k, in essentially the time required for a 6800 μ P to divide once. In the worst case, that time equals 514 CPU

clock cycles.

The routine stores the original number in HIBYTE and LOBYTE, then successively interpolates the square root two bits at a time. It begins with the number's two most significant digits and works its way down to the two least significant bits on its eighth and final loop. Accumulator A contains the running estimate, which after the last iteration represents the number's exact square root. **EDN**

Address	Op	Op	Op	Op
0000	HIBYTE	RMB	1	
0001	LOBYTE	RMB	1	
0002	DEVISR	RMB	1	
0003	COUNT	RMB	1	
1000		DRG	\$1000	
1000 86 08	SQRT	LDA	A	#8
1002 97 03		STA	A	COUNT
1004 4F		CLR	A	
1005 5F		CLR	B	
1006 79 00 01	SQRT1	ROL		LOBYTE
1009 79 00 00		ROL		HIBYTE
100C 59		ROL	B	
100D 79 00 01		ROL		LOBYTE
1010 79 00 00		ROL		HIBYTE
1013 59		ROL	B	
1014 48		ASL	A	
1015 97 02		STA	A	DEVISR
1017 78 00 02		ASL		DEVISR
101A D1 02		CHP	B	DEVISR
101C 23 06		BLS		SQRT2
101E 4C		INC	A	
101F 7C 00 02		INC		DEVISR
1022 D0 02		SUB	B	DEVISR

1024 7A 00 03	SQRT2	DEC	COUNT
1027 2E DD		BBT	SQRT1
1029 3F		SVI	
		END	

NO ERROR(S) DETECTED


SYMBOL TABLE:

COUNT	0003	DEVISR	0002
SQRT	1000	SQRT1	1006
HIBYTE	0000	LOBYTE	0001
SQRT2	1024		

Interpolating two bits at a time, this routine calculates a 16-bit number's square root in no more than 514 CPU clock cycles.

SPHERE READ ONLY MEMORY BOARD

The SPHERE ROM/1 board is designed to provide up to 4K of read only memory program space using the commonly available 1702 PROM. The addressing on the board is fully selectable on 1K boundaries by the user. All four banks must be either address strapped or grounded - no banks' address select logic may be left open. If the addressing on your board will change frequently a 14 pin DIP socket may be installed at J1-J4 and 2 inch wire-wrap type wires in the adjoining connecting holes. These wires may then be pushed into the correct hole of J1-J4

 

To select an address, jumper each connection hole to the appropriate address selection hole. To make a 'don't care' bit (either on or off will do) leave the jumper wire from the connection hole open (no connection). It is for this reason that unused banks must be strapped down.

To select 1000 as the starting address of bank 1 (U13 1000, U12 1100, U11 1200, U10 1300) connect

- 15 to address inverted, pin 1 of J1
- 14 to address inverted, pin 2 of J1
- 13 to address inverted, pin 3 of J1
- 12 to address true, pin 11 of J1
- 11 to address inverted, pin 5 of J1
- 10 to address inverted, pin 6 of J1

To select DC00 as the starting address of bank 3 (U25 DC00, U24 DD00, U23 DE00, U22 DF00) connect

- 15 to address true, pin 14 of J3
- 14 to address true, pin 13 of J3
- 13 to address inverted, pin 3 of J3
- 12 to address true, pin 11 of J3
- 11 to address true, pin 10 of J3
- 10 to address true, pin 9 of J3

To strap a bank of ROM off, connect any (at least one) connection hole to a ground, available feed-throughs near pin 7 of U9, U15, and U21.




In selecting addresses, remember that below 1000 is dedicated to RAM and above E000 are I/O devices and system ROM's.

Good programming to you all.





Ernest Dixon

Ernie Dixon
SPHERE Corporation


CHANGE NOTES

  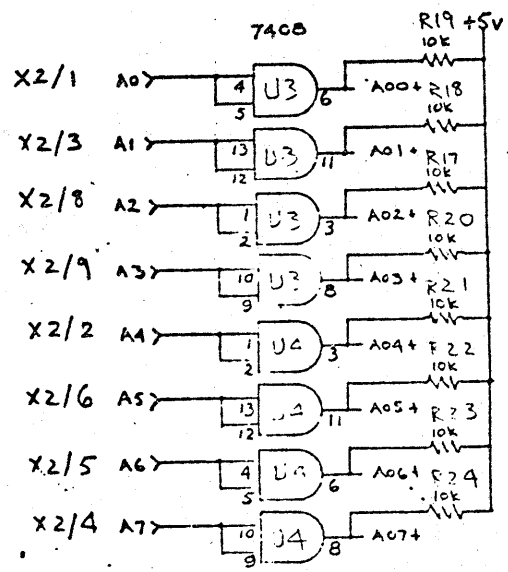

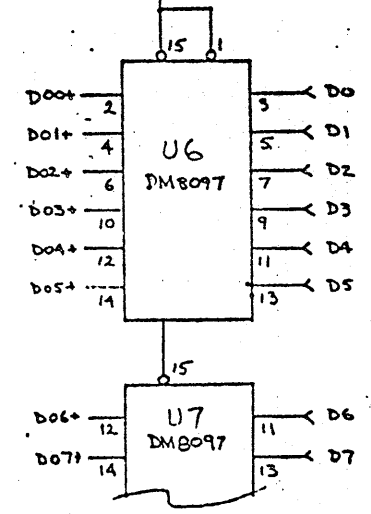 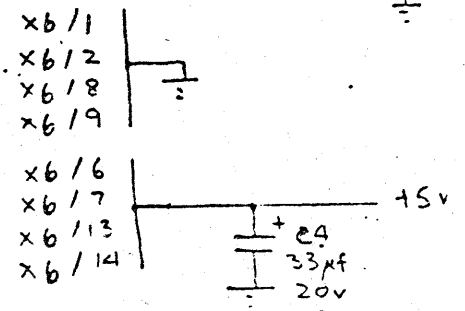 
1. C1, C2, C3, C6, C8, C9, C10
BYPASS +5V-GND
2. C7, C11, C12
BYPASS -9V-GND



RCM/1

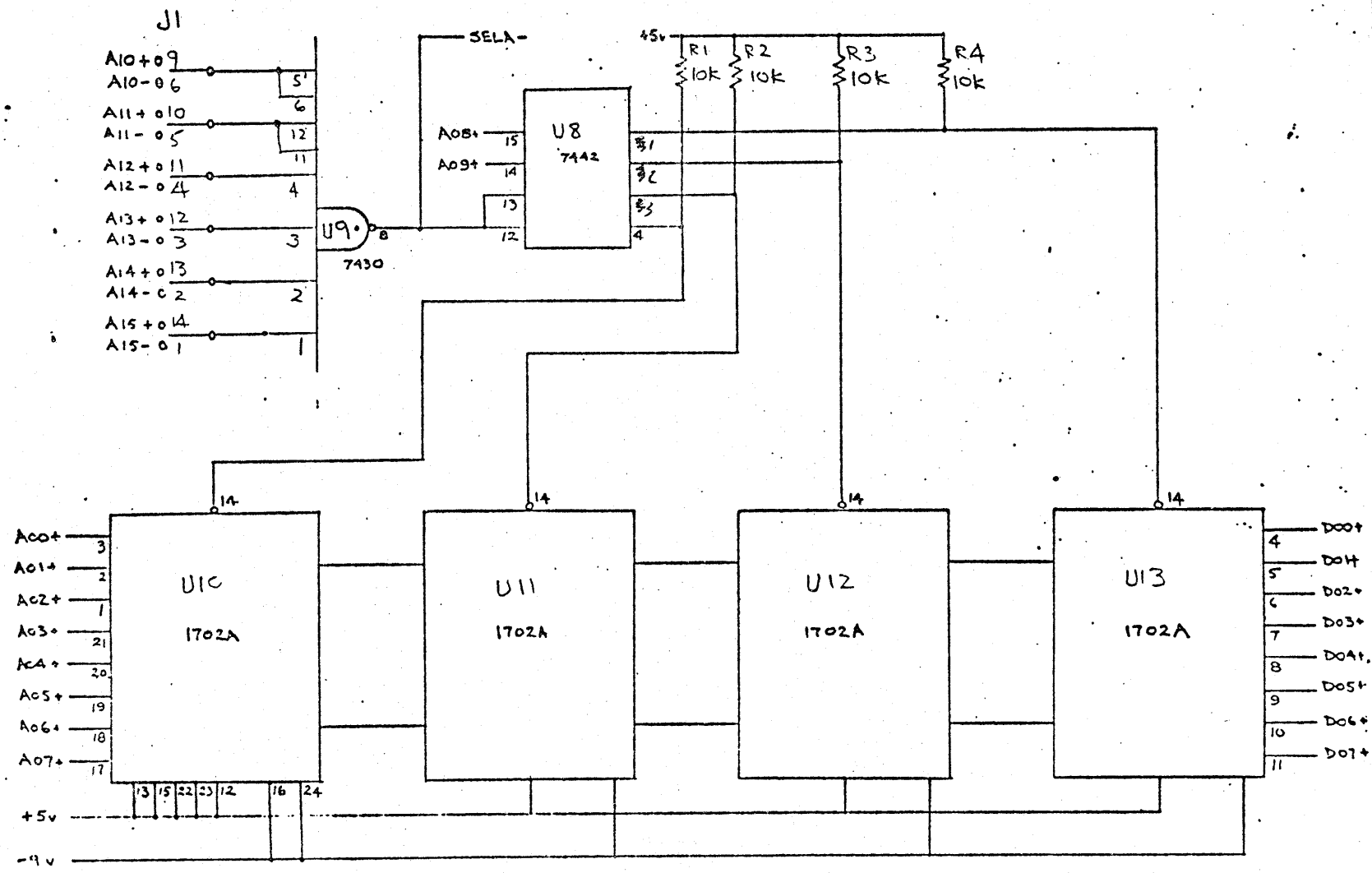


CHANGE NOTES

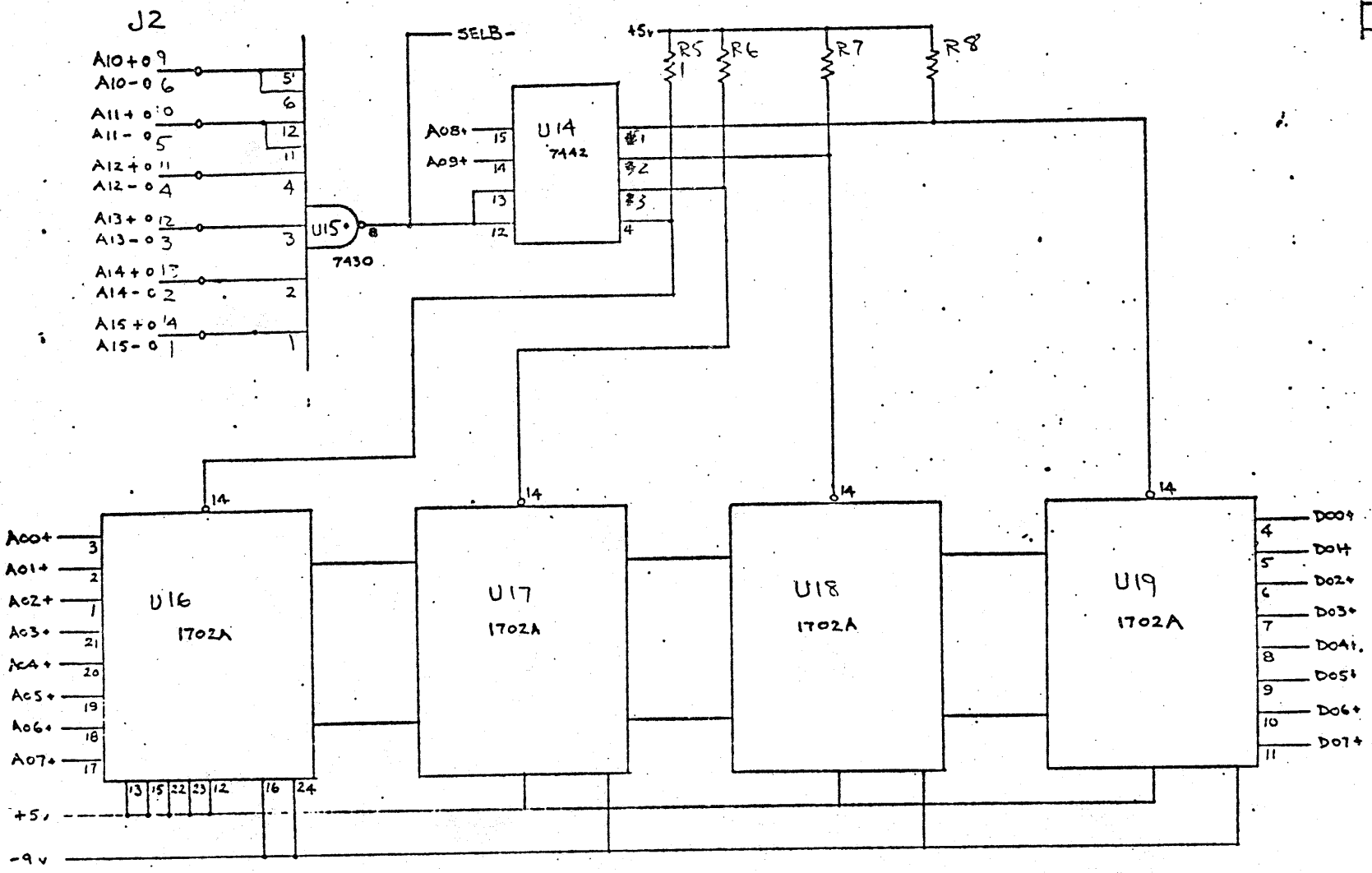


-21-

CHANGE NOTES

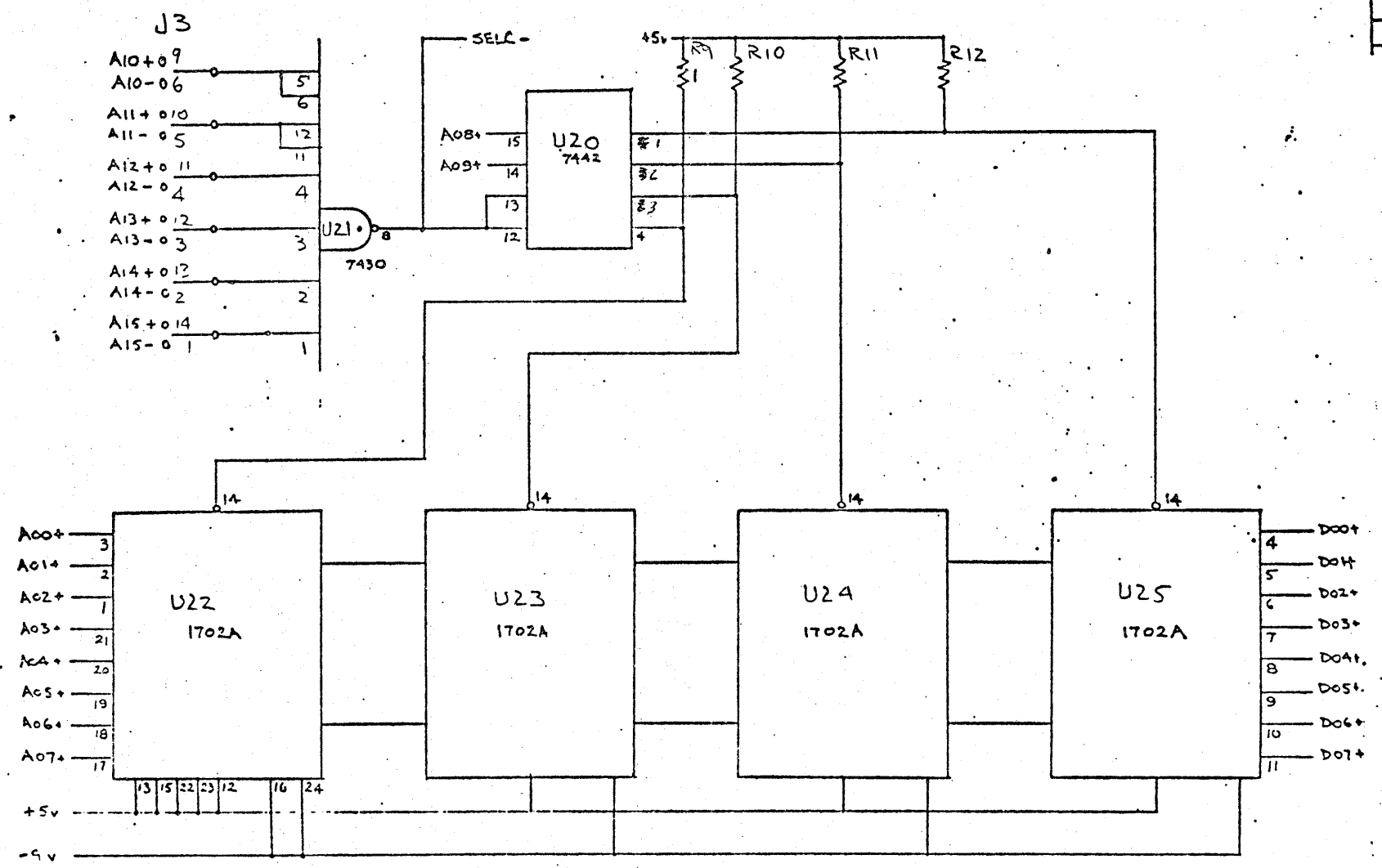

CHANGE NOTES

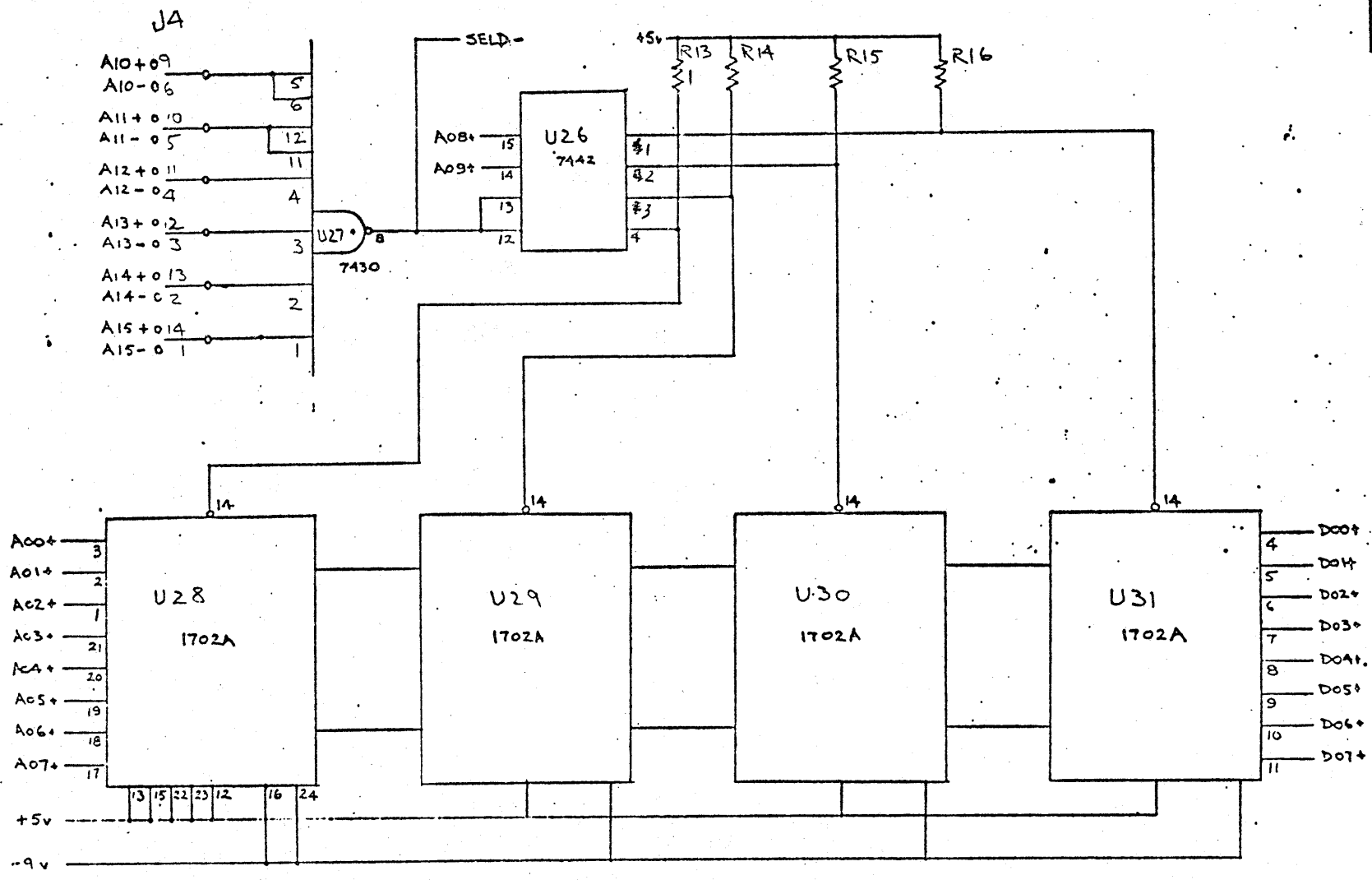

-23-


































X1

X2

X3

C4

X6

                                 

PARTS FOR ROW/1 EHD (PCB ASSY)

#	QTY	TYPE	DESCRIPTION	LOC
1	2	7404	IC HEX INVERTER	U1, U2
2	2	7408	2-IMP IC QUAD, AND	U3, U4
3	1	7420	4-IMP IC DUAL, NAND	U5
4	4	7430	IC 8-IMP NAND	U9, U15, U21, U27
5	4	7442	IC 4-10 DECODER	U8, U14, U20, U26
6	2	DM8097	IC HEX BUS DRIVER	U6, U7
7	<u>16</u>	1702A	IC 256X8 PROM	<u>U(10-13)</u> , <u>U(16-19)</u> , <u>U(22-25)</u> , <u>U(28-31)</u>
8	4	1N4001	50V RECTIFIER DIODE	D1, D2, D3, D4
9	2	33μF/20V	CAPACITOR, ELECTROLYTIC	C4, C5
10	10	0.1 μF/50V	CAPACITOR, CERAMIC	C1, C2, C3, C(6-12)
11	24	4.7K, 1/4W, 10%	RESISTOR, CARBON COMP	R(1-24)
12	4, <u>4</u>	14-pin sockets (DIP)		X1, X2, X3, X <u>6</u> , (<u>J1, J2, J3, J4</u>)
13	1	ROW/1 EHD	PCB	
14	16	24-pin DIP sockets		U(10-13), U(16-19), U(22-25), U(28-31)

UNDERLINED ITEMS NOT SUPPLIED

The Sort Routine

The Basic interpreter ^{CAN Be} ~~is~~ equipped with an alphabetic sort command which should prove useful in business applications. One can sort 250 names in ten seconds. Full 16 bit arithmetic is used so you could theoretically sort 64,000 one bit strings.

The command name is SORT

You must dimension your array on the first line of the program.
ie: 10 DIM A\$(100) To sort 100 items

The default string length is 32 bytes. Do not declare string= if you plan to use less than 32 bytes. You must use STRING= if you plan to use longer strings (max 128 bytes)

Jeff's Sort Enhancement

```

DE 22      Save STRAR
DF FE
DE 2C      GET BASIC POINTER
BD 0609    READ VARIABLE OFF LINE
DE 42      POINT TO LOCATION WHICH
09         HOLDS LOCATION IN
09         TABLE
EE 0C      GET LOCATION in X
DF 22      PUT IN 22
BD ROGER'S SORT
DE FE      RESTORE ORIGINAL 22
DF 22
39         EXIT

```

Comments about the sort: I tried Roger's sort out and found that it worked fast and well. Basic limited the number of strings that could be sorted at once to 256. To make the sorting better and to permit other arrays to be sorted in the same program, I wrote a mod of the thing. With my addition, you call your array as follows: SORT A\$(1). You can have many arrays sorted; call them by their first member! The DIM does not any longer have to be on the first line of the program.

Jeff

1		0000		NAM	SMSORT-ROGER J. SPOTT APRIL 1981	
2		0000		OPT	PNT,XRF	
3				*		
4				*	SHELL-METZNER SORT FOR CSS BASIC	
5				*		
6		0000		MDATA	EQU	X'BO'
7		0000		KDATA	EQU	X'B2'
8		0000		JDATA	EQU	X'B4'
9		0000		IDATA	EQU	X'B6'
10		0000		LDATA	EQU	X'B8'
11		0000		SADDI	EQU	X'BA'
12		0000		SADDL	EQU	X'BC'
13		0000		STPTR	EQU	X'BE'
14		0000		STRST	EQU	X'CO'
15		0000		CNTR	EQU	X'C2'
16		0000		ATEMP	EQU	X'C4'
17		0000		STRLN	EQU	X'46'
18		0000		STRAR	EQU	X'22'
19		0000		ARA	EQU	X'06'
20		0000		DIVIDE	EQU	X'FFAF'
21		0000		MULTY	EQU	X'FF93'
22				*		
23				*	SHELL-METZNER SORT FOR CSS BASIC	
24				*		
25	4R	0000	DE 06	START	LDX	ARA
26	9	0002	DF C4		STX	ATEMP
27	11	0004	5F		CLRB	
28	13	0005	0C		CLC	
29	16	0006	96 46		LDAA	STRLN
30	19	0008	9B 23		ADDA	STRAR+1
31	23	000A	97 C1		STAA	STRST+1
32	26	000C	D9 22		ADCB	STRAR
33	30	000E	D7 C0		STAB	STRST
34	34	0010	DE 22		LDX	STRAR
35	39	0012	A6 02		LDAA	02,X
36	44	0014	E6 03		LDAB	03,X
37	48	0016	97 B1		STAA	MDATA+1
38	52	0018	D7 B0		STAB	MDATA
39	54	001A	86 02	POS1	LDAA	#2
40	60	001C	7F 0006		CLR	ARA
41	64	001F	97 07		STAA	ARA+1
42	67	0021	96 B1		LDAA	MDATA+1
43	70	0023	D6 B0		LDAB	MDATA
44	79	* 0025	BD FFAF		JSR	DIVIDE
45	83	0028	97 B1		STAA	MDATA+1
46	87	002A	D7 B0		STAB	MDATA
47	93	002C	7D 00B0		TST	MDATA
48	97	002F	26 0A		BNE	GETK
49	6R	0031	7D 00B1		TST	MDATA+1
50	10	0034	26 05		BNE	GETK
51	4R	0036	DE C4		LDX	ATEMP
52	9	0038	DF 06		STX	ARA
53	14	003A	39		RTS	
54	18	003B	DE 22	GETK	LDX	STRAR
55	23	003D	A6 02		LDAA	02,X
56	28	003F	E6 03		LDAB	03,X
57	30	0041	0C		CLC	
58	33	0042	90 B1		SUBA	MDATA+1
59	36	0044	D2 B0		SBCB	MDATA
60	40	0046	97 B3		STAA	KDATA+1
61	44	0048	D7 B2		STAB	KDATA
62	50	004A	7F 00B4		CLR	JDATA
63	56	004D	7F 00B5		CLR	JDATA+1

GET STRING LENGTH
ADD IT TO START LOC.
STORE LSB
ADD WITH CARRY
STORE MSB
GET NUMBER OF ENTRIES (N)

DIVIDE M BY 2

DOES M=0?
NO, GO ON

FOR K=N-M GET K


SUBTRACT M

65	66	0053 DE B4	POS2	LDX	JDATA	
66	71	0055 DF B6		STX	IDATA	LET I=J
67	75	0057 20 '62		BRA	POS3	
68	79	0059 20 BF (001A)	POS11	BRA	POS1	
69	3R	005B 96 B1	POS3	LDAA	MDATA+1	
70	6	005D D6 B0		LDAB	MDATA	GET M
71	6	005F 0C		CLC		
72	11	0060 9B B7		ADDA	IDATA+1	ADD IT TO I
73	14	0062 D9 B6		ADCB	IDATA	
74	18	0064 97 B9		STAA	LDATA+1	STORE IT IN L
75	22	0066 D7 B8		STAB	LDATA	
76	25	0068 96 46		LDAA	STRLN	COMPUT ADDR.FOR L STR.
77	29	006A 97 07		STAA	ARA+1	
78	32	006C 96 B9		LDAA	LDATA+1	
79	35	006E D6 B8		LDAB	LDATA	
80	44 *	0070 BD FF93		JSR	MULTY	
81	47	0073 90 46		SUBA	STRLN	
82	49	0075 C2 00		SBCB	#00	
83	51	0077 0C		CLC		
84	54	0078 9B C1		ADDA	STRST+1	
85	58	007A 97 ED		STAA	SADDL+1	
86	61	007C D9 C0		ADCB	STRST	
87	65	007E D7 BC		STAB	SADDL	
88	68	0080 96 46		LDAA	STRLN	COMPUT ADDR.FOR I STRING
89	74	0082 7F 0006		CLR	ARA	
90	78	0085 97 07		STAA	ARA+1	
91	81	0087 96 B7		LDAA	IDATA+1	
92	84	0089 D6 B6		LDAB	IDATA	
93	93 *	008B BD FF93		JSR	MULTY	
94	96	008E 90 46		SUBA	STRLN	
95	98	0090 C2 00		SBCB	#00	
96	100	0092 0C		CLC		
97	103	0093 9B C1		ADDA	STRST+1	
98	107	0095 97 BB		STAA	SADDI+1	
99	110	0097 D9 C0		ADCB	STRST	
100	114	0099 D7 BA		STAB	SADDI	
101	118	009B 20 17		BRA	COMP	
102	2R	009D 5F	POS4	CLRB		
103	4	009E 86 01		LDAA	#01	
104	7	00A0 9B B5		ADDA	JDATA+1	
105	10	00A2 D9 B4		ADCB	JDATA	
106	14	00A4 97 B5		STAA	JDATA+1	
107	18	00A6 D7 B4		STAB	JDATA	
108	21	00A8 D1 B2		CMPB	KDATA	
109	25	00AA 22 AD (0059)		BHI	POS11	
110	3R	00AC 91 B3		CMPA	KDATA+1	
111	7	00AE 22 A9 (0059)		BHI	POS11	
112	11	00B0 20 A1 (0053)		BRA	POS2	
113	15	00B2 20 A7 (005B)	POS13	BRA	POS3	
114	3R	00B4 D6 46	COMP	LDAB	STRLN	COUNTER STRING LENGTH
115	7	00B6 DE BC		LDX	SADDL	ADDR. OF L INTO INDEX REG
116	12	00B8 9F BE		STS	STPTR	SAVE STACK
117	16	00BA 9E BA		LDS	SADDI	ADDRESS OF I INTO STACK
118	20	00BC 34		DES		POSITION STACK
119	24	00BD 32	NEXT	PULA		GET FIRST CHAR. OF STRING
120	29	00BE A1 00		CMPA	00,X	COMPARE TO 1ST IN IND.REG
121	33	00C0 26 06		BNE	TEST	FIND OUT WHICH IS BIGGER
122	2R	00C2 5A		DECB		TEST NEXT CHARACTER
123	6	00C3 27 05		BEQ	RESTR	END OF STRING
124	4R	00C5 08		INX		
125	8	00C6 20 F5 (00BD)		BRA	NEXT	
126	12	00C8 22 04	TEST	BHI	EXCH	I>L SWITCH PLACES
127	4R	00CA 9E BE	RESTR	LDS	STPTR	NO SWITCH


Sort Contd

129	3R	00CE	96 46	EXCH	LDAA	STRLN	GET STRING LENGTH
130	7	00D0	97 C2		STAA	CNTR	PUT INTO COUNTER
131	11	00D2	DE BA		LDX	SADDI	1ST STRING ADDRESS (I)
132	15	00D4	9E BC		LDS	SADDL	2ND STRING ADDRESS(L)
133	19	00D6	34		DES		
134	23	00D7	32	PULL	PULA		GET 1ST CHARACTER INTO A
135	28	00D8	E6 00		LDAB	00,X	2ND CHARACTER INTO B
136	34	00DA	A7 00		STAA	00,X	PUT A WHERE B CAME FROM
137	38	00DC	08		INX		MOVE INDEX POINTER
138	42	00DD	37		PSHB		PUT B WHERE A CAME FROM
139	46	00DE	31		INS		MOVE STACK POINTER
140	52	00DF	7A 00C2		DEC	CNTR	
141	56	00E2	26 F3 (00D7)		BNE	PULL	NOT DONE YET
142	4R	00E4	9E BE		LDS	STPTR	RESET STACK
143	7	00E6	96 B7		LDAA	IDATA+1	
144	10	00E8	D6 B6		LDAB	IDATA	
145	13	00EA	D1 B0		CMFB	MDATA	
146	17	00EC	22 06		BHI	SUB	
147	21	00EE	27 02		BEQ	LSB	
148	25	00F0	20 AB (009D)		BRA	POS4	
149	3R	00F2	91 B1	LSB	CMFA	MDATA+1	
150	7	00F4	22 04		BHI	SUB	
151	11	00F6	27 BA (00B2)		BEQ	POS13	
152	15	00F8	20 A3 (009D)		BRA	POS4	
153	2R	00FA	0C	SUB	CLC		
154	5	00FB	90 B1		SUBA	MDATA+1	
155	8	00FD	D2 B0		SBCB	MDATA	
156	12	00FF	D7 B6		STAB	IDATA	
157	16	0101	97 B7		STAA	IDATA+1	
158	20	0103	20 AD (00B2)		BRA	POS13	
159		0105			END		

BA TRIGGERS NMI (Ignores Refresh)

 

OR

 

use Schmitt trigger 74LS14 or 74LS13

THIS PROGRAM WILL PROVIDE A PITCH AT LINE Ø FROM THE PIA WHICH CORRESPONDS TO THE KEY PUSHED, ANY KEY OF THE MIDDLE ROW. IF I REMEMBER CORRECTLY, "A" (the key) GIVES A FAIRLY LOW MUSICAL "C", S GIVES C#, D GIVES THE NOTE D, F GIVES D#, ETC. THEY ARE ALL USED UP AND INCLUDING THE VERTICAL LINE, BUT NOT DELETE.

```

2000 B6 LDA A $F043
R20E2G
> 2003 84 AND A #$FB ..
> 2005 B7 STA A $F043 ..C
> 2008 86 LDA A #$01 ..
> 200A B7 STA A $F042 ..B
> 200D B6 LDA A $F043 ..C
> 2010 8A ORA A #$04 ..
> 2012 B7 STA A $F043 ..C To here, initialize PIA
> 2015 F6 LDA B $F041 ..A key test ( should say, key down test)
> 2018 C5 BIT B #$40 ..e
> 201A 27 BEQ $F9 2015 '.
> 201C F6 LDA B $F040 ..g Load from PIA which key was pressed
> 201F D7 STA B $C0 ..
> 2021 20 BRA $02 2025 ..
> 2023 20 BRA $F0 2015 .. (island)
> 2025 C1 CMP B #$7C .. (Is it the rightmost key- vertical line)
> 2027 26 BNE $05 202E &.
> 2029 CE LDX #$0046 ..F Yes? LDX 46
> 202C 20 BRA $6E 209C .. And go to tone generator
> 202E C1 CMP B #$7E .. Is it tilda?
> 2030 26 BNE $05 2037 &.
> 2032 CE LDX #$004A ..J if so, LDX w/ 4A
> 2035 20 BRA $65 209C .. and go to tone generator
> 2037 C1 CMP B #$3A ..: Colon
> 2039 26 BNE $05 2040 &.
> 203B CE LDX #$004F ..0 LDX w/ 4F ( the higher the #, the longer it takes
> 203E 20 BRA $5C 209C .\ to count down, so the lower the pitch)
> 2040 C1 CMP B #$3B ..;
> 2042 26 BNE $05 2049 &.
> 2044 CE LDX #$0054 ..T
> 2047 20 BRA $53 209C .S
> 2049 C1 CMP B #$4C ..L
> 204B 26 BNE $05 2052 &.
> 204D CE LDX #$0059 ..Y (G#)
> 2050 20 BRA $4A 209C .J
> 2052 C1 CMP B #$4B ..K
> 2054 26 BNE $05 205B &.
> 2056 CE LDX #$005F ..- (G)
> 2059 20 BRA $41 209C .A
> 205B C1 CMP B #$4A ..J
> 205D 26 BNE $05 2064 &.
> 205F CE LDX #$0064 ...
> 2062 20 BRA $38 209C .8
> 2064 C1 CMP B #$48 ..H
> 2066 26 BNE $05 206D &.
> 2068 CE LDX #$006A ...
> 206B 20 BRA $2F 209C ./
> 206D C1 CMP B #$47 ..G
> 206F 26 BNE $05 2076 &.
> 2071 CE LDX #$0071 ...
> 2074 20 BRA $26 209C .&
> 2076 C1 CMP B #$46 ..F
> 2078 26 BNE $05 207F &.
> 207A CE LDX #$0077 ...

```

Musical Tone Generator Cont'd

```

> 207D 20 BRA $1D 209C ..
> 207F C1 CMP B #$44 .D
> 2081 26 BNE $05 2088 &.
> 2083 CE LDX #$0080 ...
> 2086 20 BRA $14 209C ..
> 2088 C1 CMP B #$41 .A
> 208A 26 BNE $05 2091 &.
> 208C CE LDX #$0090 ...
> 208F 20 BRA $0B 209C ..
> 2091 C1 CMP B #$53 .S
> 2093 26 BNE $05 209A &.
> 2095 CE LDX #$0089 ...
> 2098 20 BRA $02 209C ..
> 209A 20 BRA $87 2023 ..
> 209C DF STX $C1 ..
> 209E DE LDX $C1 ..
> 20A0 B7 STA A %F042 ..B
> 20A3 09 DEX .
> 20A4 26 BNE $FD 20A3 &.
> 20A6 88 EOR A #$01 ..
> 20A8 F6 LDA B %F040 ..@
> 20AB D1 CMP B $C0 ..
> 20AD 27 BEQ $EF 209E ..
> 20AF 7E JMP %201C ...

```

Begin the tone generator - store the starting no.

Store A in the PIA - output
DEC X

If A were high, go low, if low, go high; switches
to form square wave output.

```


B6 F0 43 84 FE B7 F0 43 86 01 B7 F0 42 B6 F0 43
8A 04 B7 F0 43 F6 F0 41 C5 40 27 F9 F6 F0 40 D7
C0 20 02 20 F0 C1 7C 26 05 CE 00 46 20 6E C1 7E
26 05 CE 00 4A 20 65 C1 3A 26 05 CE 00 4F 20 5C
C1 3B 26 05 CE 00 54 20 53 C1 4C 26 05 CE 00 59
20 4A C1 6B 26 05 CE 00 5F 20 41 C1 4A 26 05 CE
00 64 20 38 C1 48 26 05 CE 00 6A 20 2F C1 47 26
05 CE 00 71 20 26 C1 46 26 05 CE 00 77 20 1D C1
44 26 05 CE 00 80 20 14 C1 41 26 05 CE 00 90 20
0E C1 53 26 05 CE 00 89 20 02 20 87 DF C1 DE C1
B7 F0 52 09 26 FD 88 01 F6 F0 40 D1 C0 27 EF 7E
20 1C 00

```


3.0 SOFTWARE ARCHITECTURE

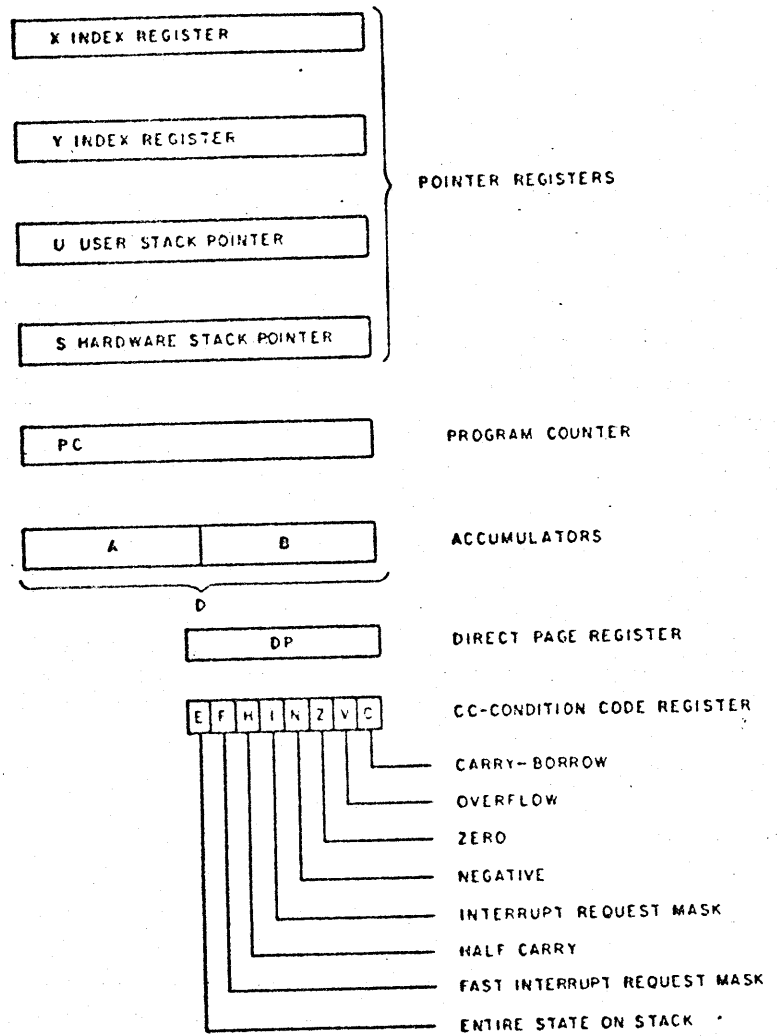3.1 6809 PROGRAMMING MODEL

The 6809 contains four 8-bit registers and five 16-bit registers which are visible to the programmer:



The Double-Accumulator D consists of the two 8-bit accumulators concatenated A:B. The A-register is the MS byte of the pair while the B-register is the LS byte.

3.1.1 Accumulators (A, B & D)

The A and B registers are general purpose accumulators used for arithmetic calculations and data manipulation. With the exception of ABX, DAA and 16-bit operations, the two accumulators are completely interchangeable. In the catenated form the A-register is the MS byte of the pair thru forming the 16-bit Double Accumulator, or D-register.

3.1.2 Direct Page Register (DP)

The Direct Page register defines the MS byte to be used in the direct mode of addressing; the DP is catenated with the byte following the direct-mode op code to form a 16-bit effective address. The DP will be initialized to \$00 by RESET for 6800 compatibility.

3.1.3 Condition Code Register (CC)

The Condition Code register defines the state of the processor flags at any given time. The bits in the CC are:

B7	B6	B5	B4	B3	B2	B1	B0
E	F	H	I	N	Z	V	C

Bit 5 and bits 3-0 are set as the result of instructions that manipulate data; for details, see condition code section for each instruction.

3.1.4 Index Register (X, Y)

The index registers are used in indexed mode addressing. They provide a 16-bit address to be added to an optional offset (of up to 16-bits) for indexed instructions; the result of the addition is the effective address of the instruction. For more details see the section on addressing modes. The X and Y registers are essentially equivalent in usage and support the same instructions. Because automatic pre-increment and post-decrement options are available on indexed-mode operations, these registers may be used to easily implement software stacks, queues, and buffers.

3.1.5 Stack Pointers (U , S)

The stack pointer registers contain addresses that point to the top of a push-down/pop-up stack. Data and machine state can be pushed onto the stack (stored at the next memory address to that "pointed" to by the U or S) or pulled from the stack in a last-in first-out manner. Pushes decrement the stack pointer before the data is stored while pulls increment the stack pointer after the data is recovered; the stack pointers point at the last byte placed on the stack. The S is used by the hardware to automatically store subset or entire machine states during subroutines and interrupts. The User Stack (U) is controlled exclusively by the programmer and can be used to pass arguments to and from subroutines. Both the U and S have the same indexed-mode addressing capabilities as

3.1.5 (Continued)

the X and Y index registers; the stack pointers are enhanced index registers (although the operation as LEA is slightly different on the stack registers). This allows the 6809 to be used efficiently as a stack processor, greatly enhancing its ability to support higher level languages.

3.1.6 Program Counter (PC)

The PC is used by the hardware to point to the next instruction to be executed by the processor. Limited indexed-mode addressing is available on the PC (i.e., auto-increment/decrement is not available). For notational convenience the description of each instruction assumes that the program counter points one location past the last byte of the op code, as it would after decoding the instruction. As additional bytes are used by the instruction the PC always points to the next unused byte.

EXAMPLE: The branch instructions are available in either short or long forms; in general the short form takes a one-byte opcode, while the long form takes two bytes. After decoding the opcode, the PC points at either a one- (short branch) or two-byte (long) immediate value, which is taken into the machine for addition to the PC. If the branch is not taken, the addition never happens and the PC remains pointing to the next instruction. Indexed-mode instructions also have variable length fields.

6809 INDEXED ADDRESSING

TYPE	FORMS	NON - INDIRECT				INDIRECT			
		SOURCE	POST-BYTE	~	#	SOURCE	POST-BYTE	~	#
CONSTANT OFFSET FROM R	NO OFFSET	,R	IRR00100	0	0	[,R]	IRR10100	3	0
	5-BIT OFFSET	n,R	ORRnnnnn	1	0	defaults to 8-bit			
	8-BIT OFFSET	n,R	IRR01000	1	1	[n,R]	IRR11000	4	1
	16-BIT OFFSET	n,R	IRR01001	4	2	[n,R]	IRR11001	7	2
ACCUMULATOR OFFSET FROM R	A-REGISTER OFFSET	A,R	IRR00110	1	0	[A,R]	IRR10110	4	0
	B-REGISTER OFFSET	B,R	IRR00101	1	0	[B,R]	IRR10101	4	0
	D-REGISTER OFFSET	D,R	IRR01011	4	0	[D,R]	IRR11011	7	0
AUTO-INCREMENT/ -DECREMENT R	INCREMENT BY 1	,R+	IRR00000	2	0	not allowed			
	INCREMENT BY 2	,R++	IRR00001	3	0	[,R++]	IRR10001	6	0
	DECREMENT BY 1	,-R	IRR00010	2	0	not allowed			
	DECREMENT BY 2	,--R	IRR00011	3	0	[,--R]	IRR10011	6	0
CONSTANT OFFSET FROM PC	8-BIT OFFSET	n,PCR	IXX01100	1	1	[n,PCR]	IXX11100	4	1
	16-BIT OFFSET	n,PCR	IXX01101	5	2	[n,PCR]	IXX11101	8	2
EXTENDED		Use non-indexed			[n]	10011111	5	2	

Figure 4: Indexed Addressing Modes. All instructions with indexed addressing have a base size and number of cycles. The ~ and # columns indicate the number of additional cycles and bytes for the particular variation. The post byte opcode is the byte that immediately follows the normal opcode.


-361

3.12 INDEXED-MODE POST-BYTE

POST BYTE REGISTER

BIT ASSIGNMENTS

POST-BYTE REGISTER BIT								INDEXED ADDRESSING MODE
7	6	5	4	3	2	1	0	
1	X	X	X	0	0	0	1	,R++
1	X	X	0	0	0	0	0	,R+
1	X	X	0	0	0	1	0	,-R
1	X	X	X	0	0	1	1	,--R
1	X	X	X	0	1	0	0	EA=(R ± 0 OFFSET)
1	X	X	X	0	1	0	1	EA=(R ± ACCB OFFSET)
1	X	X	X	1	0	0	0	EA=(R ± 7BIT OFFSET)
1	X	X	X	1	0	0	1	EA=(R ± 15 BIT OFFSET)
1	X	X	X	1	1	0	0	EA=(PC ± 7 BIT OFFSET)
1	X	X	X	1	1	0	1	EA=(PC ± 15 BIT OFFSET)
0	X	X	X	X	X	X	X	EA=(R ± 4 BIT OFFSET)
1	X	X	X	0	1	1	0	EA=(R ± ACCA OFFSET)
1	X	X	X	1	0	1	1	EA=(R ± D OFFSET)
1	X	X	1	1	1	1	1	EA=(ADDRESS)

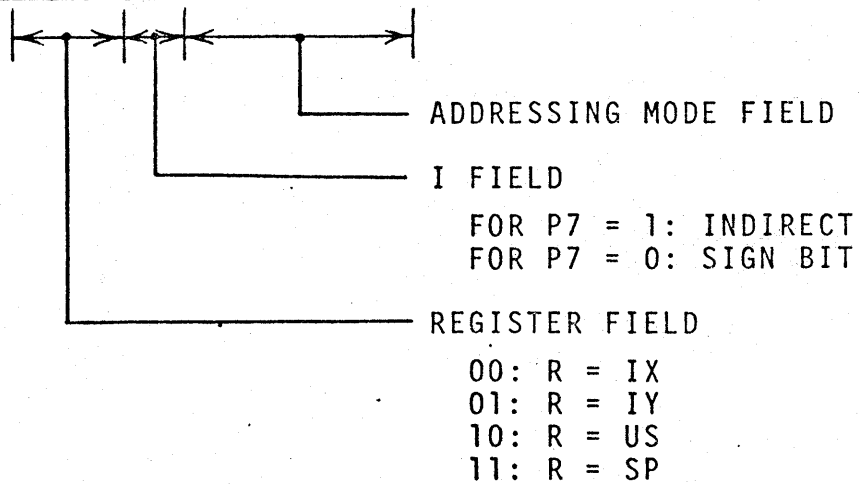

3.14 BRANCH GROUPS

Simple Conditional Branches

<u>Condition</u>	<u>Complement</u>
BEQ {Z=1}	BNE
BMI {N=1}	BPL
BCS {C=1}	BCC
BVS {V=1}	BVC

Signed Conditional Branches

<u>Condition</u>	<u>Complement</u>
BGT { $(N \oplus V) \wedge \bar{Z}=1$ }	BLE
BGE { $(N \oplus V)=1$ }	BLT
BEQ {Z=1}	BNE
BLE { $(N \oplus V) \vee Z=1$ }	BGT
BLT { $(N \oplus V)=1$ }	BGE

Unsigned Conditional Branches*

<u>Condition</u>	<u>Complement</u>
BHI { $(\bar{C} \wedge \bar{Z})=1$ }	BLS
BHS { $\bar{C}=1$ }	BLO
BEQ {Z=1}	BNE
BLS { $C \vee Z=1$ }	BHI
BLO {C=1}	BHS

* Not useful, in general, after INC/DEC, LD/ST, TST/CLR/COM.

ABX	Add B-register to X-register unsigned
ADCA,ADCB	Add memory to accumulator with carry
ADDA,ADDB	Add memory to accumulator
ANDA,ANDB	And memory with accumulator
ANDCC	And immediate with condition code register
ASLA,ASLB,ASL	Arithmetic shift left accumulator or memory
ASRA,ASRB,ASR	Arithmetic shift right accumulator or memory
BITA,BITB	Bit test memory with accumulator
CLRA,CLRB,CLR	Clear accumulator or memory
CMPA,CMPB	Compare memory with accumulator
COMA,COMB,COM	Complement accumulator or memory
DAA	Decimal Adjust A-accumulator
DECA,DECB,DEC	Decrement accumulator or memory
EORA,EORB	Exclusive or memory with accumulator
EXG R1,R2	Exchange R1 with R2
INCA,INCB,INC	Increment accumulator or memory
LDA,LDB	Load accumulator from memory
LSLA,LSLB,LSL	Logical shift left accumulator or memory
LSRA,LSRB,LSR	Logical shift right accumulator or memory
MUL	Unsigned multiply (8 bit x 8 bit = 16 bit)
NEGA,NEGB,NEG	Negate accumulator or memory
ORA,ORB	Or memory with accumulator
ORCC	Or immediate with condition code register
PSHS {register} ⁸	Push register(s) on hardware stack
PSHU {register} ⁸	Push register(s) on user stack
PULS {register} ⁸	Pull register(s) from hardware stack
PULU {register} ⁸	Pull register(s) from user stack
ROLA,ROLB,ROL	Rotate accumulator or memory left
RORA,RORB,ROR	Rotate accumulator or memory right
SBCA,SBCB	Subtract memory from accumulator with borrow
STA,STB	Store accumulator to memory
SUBA,SUBB	Subtract memory from accumulator
TSTA,TSTB,TST	Test accumulator or memory
TFR R1,R2	Transfer register R1 to register R2

FIGURE 1 8-BIT OPERATIONS

ADDD	Add to D accumulator
SUBD	Subtract from D accumulator
LDD	Load D accumulator
STD	Store D accumulator
CMPD	Compare D accumulator
LDX,LDY,LDS,LDU	Load pointer register
STX,STY,STS,STU	Store pointer register
CMPX,CMPY,CMPU,CMPS	Compare pointer register
LEAX,LEAY,LEAS,LEAU	Load effective address into pointer register
SEX	Sign Extend
TFR register,register	Transfer register to register
EXG register,register	Exchange register to register
PSHS (register) ₀	Push register(s) onto hardware stack
PSHU (register) ₀	Push register(s) onto user stack
PULS (register) ₀	Pull register(s) from hardware stack
PULU (register) ₀	Pull register(s) from user stack

FIGURE 2 16-BIT OPERATIONS

0,R	indexed with zero offset
[0,R]	indexed with zero offset indirect
,R+	auto increment by 1
,R++	auto increment by 2
[,R++]	auto increment by 2 indirect
,-R	auto decrement by 1
,--R	auto decrement by 2
[,--R]	auto decrement by 2 indirect
n,P	indexed with signed n as offset (n=5,8, or 16-bits)
[n,P]	indexed with signed n as offset indirect
A,R	indexed with accumulator A as offset
[A,R]	indexed with accumulator A as offset indirect
B,R	indexed with accumulator B as offset
[B,R]	indexed with accumulator B as offset indirect
D,R	indexed with accumulator D as offset
[D,R]	indexed with accumulator D as offset indirect

R = X, Y, U or S

P = PC, X, Y, U or S

FIGURE 3 INDEXED ADDRESSING MODES

BCC, LBCC	Branch if carry clear
BCS, LBCS	Branch if carry set
BEQ, LBEQ	Branch if equal
BGE, LBGE	Branch if greater than or equal (signed)
BGT, LBGT	Branch if greater (signed)
BHI, LBHI	Branch if higher (unsigned)
BHS, LBHS	Branch if higher or same (unsigned)
BLE, LBLE	Branch if less than or equal (signed)
BLO, LBLO	Branch if lower (unsigned)
BLS, LBLS	Branch if lower or same (unsigned)
BLT, LBLT	Branch if less than (signed)
BMI, LBMI	Branch if minus
BNE, LBNE	Branch is not equal
BPL, LBPL	Branch if plus
BRA, LBRA	Branch always
BRN, LBRN	Branch never
BSR, LBSR	Branch to subroutine
BVC, LBVC	Branch if overflow clear
BVS, LBVS	Branch if overflow set

FIGURE 4 RELATIVE SHORT AND LONG BRANCHES

CWAI	Clear condition code register bits and wait for interrupt
NOP	No-operation
JMP	Jump
JSR	Jump to subroutine
RTI	Return from interrupt
RTS	Return from subroutine
SEX	Sign extend B-register into A-register
SWI,SWI2,SWI3	Software interrupts
SYNC	Synchronize with interrupt line

FIGURE 5 MISCELLANEOUS INSTRUCTIONS